

ESD PROJECT REPORT

Electric Piano Circuit using 555 timer IC

Fourth Semester Electronics and Communication Engineering

Submitted by

Student Name: KRISH AGARWAL

Reg. No: 230907418

Student Name: VANSI ODHRANI

Reg. No: 230907434

Student Name: YUVRAJ S YALI

Reg. No: 230907440

DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING

MANIPAL INSTITUTE OF TECHNOLOGY

(A Constituent Institution of Manipal Academy of Higher Education)

MANIPAL – 576104, KARNATAKA, INDIA

JAN/MAY 2025



Abstract


This report will walk us through on how to make an Electronic Piano circuit using 555 timekeeper IC and many other electronics factors. This circuit consists of a number of drive button switches(analogous to different keys in a piano) which, when pressed, generates sounds of different frequencies via a speaker. The frequency of the affair tones can also be fine- tuned by calculating the precise values of resistors to use. This design showcases the practical operation of introductory electronic factors in sound generation

Aim/Objective

The primary objective of this experiment is to design and construct a simple piano circuit using a 555 timer IC in a stable mode, switches, a speaker, and basic passive components such as resistors and capacitors. The circuit generates different audio frequencies, corresponding to musical notes, when specific buttons are pressed.

The 555 timer IC is a versatile component used to generate square wave signals in astable mode. The output frequency is determined by the resistor and capacitor values in the RC network connected to the IC. By pressing different push buttons, the resistance in the circuit changes, altering the frequency and producing different tones through the speaker. This circuit demonstrates basic principles of frequency generation and sound synthesis.

Methodology

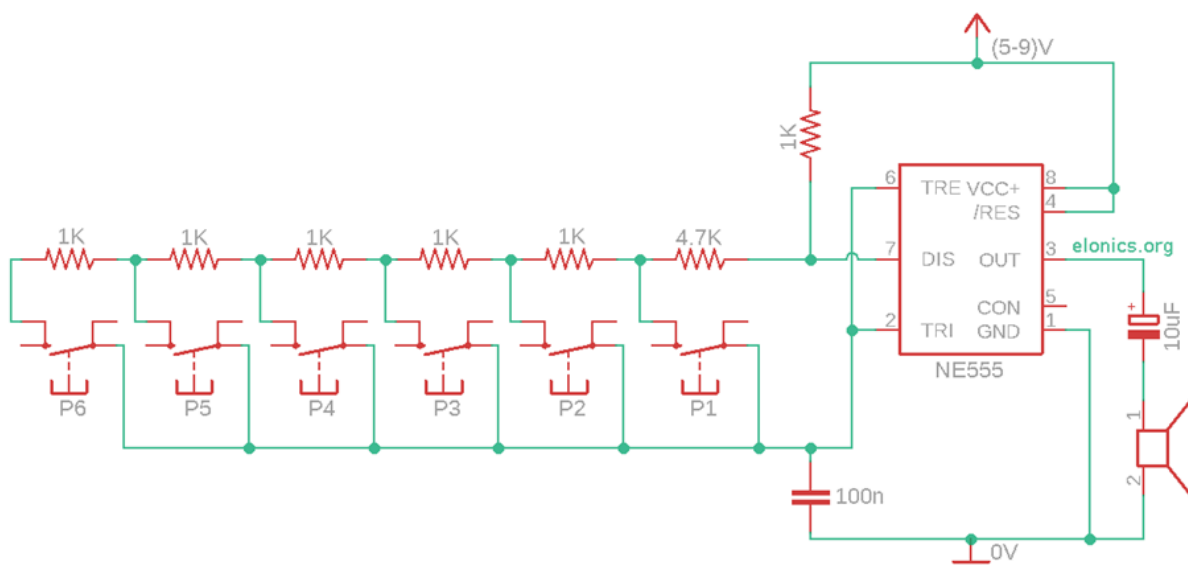

ELECTRIC PIANO CIRCUIT

Methodology

1. Planning and Design:

- Research the operation of the 555 timer IC in astable mode.
- Determine the required components and calculate resistor and capacitor values to produce desired audio frequencies.
- Sketch a preliminary circuit diagram to visualize the connections and layout.

2. Component Procurement:

- Gather the required components, ensuring they match the specifications (e.g., resistance values, capacitor ratings, and speaker impedance).
- Check the 555 timer IC and other components for proper functionality before assembly.

3. Circuit Assembly:

- Place the 555 timer IC on the breadboard and make the necessary connections as per the circuit diagram.
- Connect the RC network with the appropriate resistor and capacitor values to Pins 2, 6, and 7 of the IC.
- Attach push buttons in series with individual resistors to enable tone selection.
- Connect the output (Pin 3) to the speaker through a current-limiting resistor.

4. Testing and Calibration:

- Power the circuit using a 9V battery and verify that the connections are secure.
- Press each push button individually to test the output tones.
- Use an oscilloscope to measure the output frequency and compare it with calculated values.
- Adjust resistor or capacitor values if the tones deviate significantly from the desired frequencies.

5. Data Collection:

- Record the frequencies and tones produced for each button press.
- Document any discrepancies and note potential causes, such as component tolerances or connection issues.

6. Analysis and Optimization:

- Analyze the recorded data to confirm that the circuit meets the objective of generating distinct tones.
- Optimize the circuit layout for clarity and reliability.
- Implement improvements, such as replacing fixed resistors with potentiometers for finer control of frequencies.

Working

1. The circuit operates by utilizing the 555 timer IC in astable mode to generate continuous square wave signals.
2. When power is supplied to the circuit, the capacitor connected between Pin 2/6 and GND begins to charge and discharge through the resistors.
3. The charging and discharging cycles create a repetitive voltage fluctuation at Pins 2 and 6, which triggers the 555 timer IC to output a square wave signal at Pin 3.
4. The frequency of the output signal is determined by the resistor and capacitor values in the RC network. Each push button is connected to a specific resistor value, altering the total resistance in the circuit when pressed.
5. Pressing a button changes the resistance, modifying the charge and discharge rate of the capacitor and thus altering the frequency of the output signal.
6. The output signal from Pin 3 drives the speaker, converting the electrical square wave into audible sound. Each button press produces a distinct frequency, corresponding to a musical tone.

Components Required

- 555 Timer IC
- 8 Ohm Speaker
- 6 x Momentary Push Button Switches
- Capacitors: 100nF, 10uF
- Resistors: 6 x 1K, 4.7K
- Breadboard
- Few Breadboard Connectors
- (5-9)V Power Supply

Results

The piano circuit successfully generated distinct tones corresponding to different button presses. The frequency of each tone was consistent with the theoretical calculations.

The experiment demonstrated the use of the 555 timer IC in astable mode for generating audio frequencies. By varying the resistance in the circuit through push buttons, different tones were achieved. This project showcases the practical application of basic electronic components in sound generation. The experiment demonstrated the use of the 555 timer IC in astable mode for generating audio frequencies. By varying the resistance in the circuit through push buttons, different tones were achieved. This

project showcases the practical application of basic electronic components in sound generation.

References

- *DIY Electric Piano Circuit using 555 timer IC*

[DIY Electric Piano Circuit using 555 timer IC](#)

- *DIY Electronic Piano Circuit on Breadboard*

 [DIY Electronic Piano Circuit on Breadboard | 555 Timer Project #9](#)

- *Electronic Piano Circuit Using 555 timer IC*

[Electronic Piano Circuit Using 555 timer IC](#)